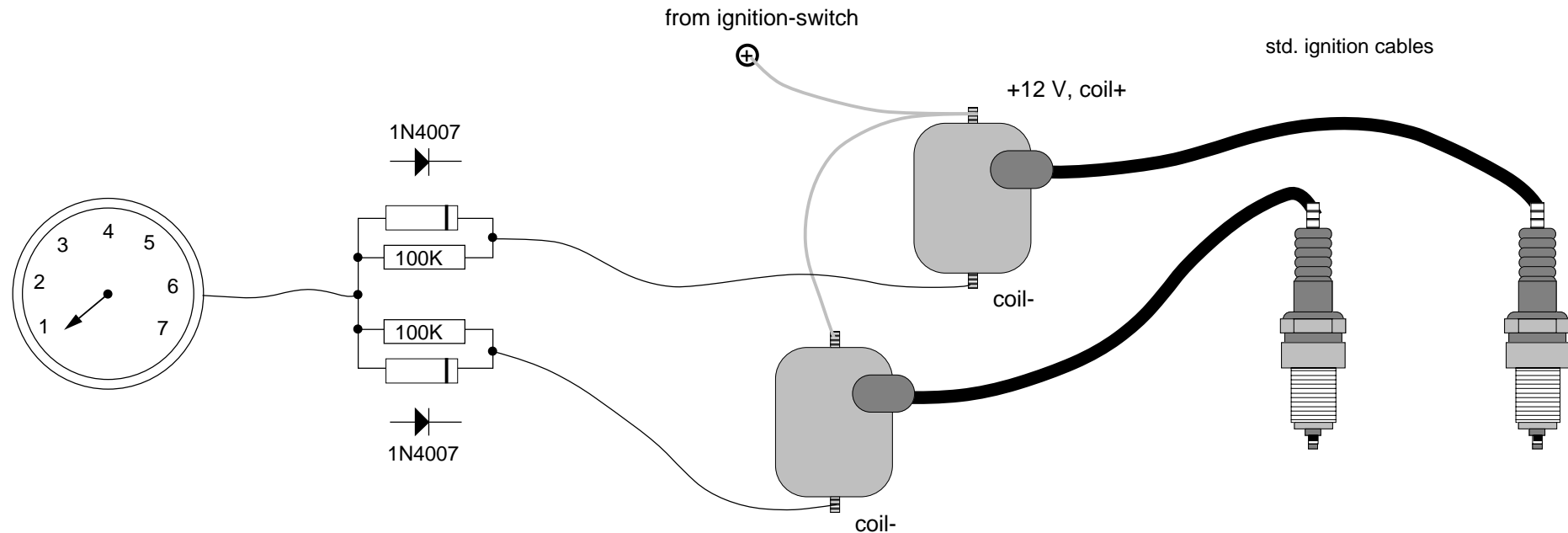


Simple rev adapter (single-fire)

30/5/98

If you have a single-fire ignition system, and your tach shows only 1/2 of the actual rpm, you may use this simple circuit for correct rpm-display (cost: just a few cents). Use shrinking tube for isolation of the components.

You need 2 resistors 100 K-OHM and 2 diodes 1N4007 (radio-shack).



ATTENTION: May not function with every ignition / tachometer. Use at own risk.